 


11. 4-bit BARREL SHIFTER (only left rotate)

- they are digital circuits (not sequential i.e. no flip flops used)
- we use MUX (combinational)
- to shift/rotate bits
- both left/right



CODE:

```
`timescale 1ns / 1ps
```

```
module barrel_shifter(
```

```
    input [3:0] w,
```

```
    input [1:0] s,
```

```
    output [3:0] y
```

```
);
```

```
    mux4x1 m0(w[3],w[0],w[1],w[2], s, y[3]);
```

```
    mux4x1 m1(w[2],w[3],w[0],w[1], s, y[2]);
```

```
    mux4x1 m2(w[1],w[2],w[3],w[0], s, y[1]);
```

```
    mux4x1 m3(w[0],w[1],w[2],w[3], s, y[0]);
```

```
endmodule
```

```
module mux4x1(
```

```
    input i0,i1,i2,i3,
```

```
    input [1:0]s,
```

```
    output reg y
```

```
);
```

```
always@(*)begin
```

```

case(s)
  2'b00: y = i0;
  2'b01: y = i1;
  2'b10: y = i2;
  2'b11: y = i3;
  default: y = 4'b0;
endcase
end
endmodule

//testbench

`timescale 1ns / 1ps


module tb_bs;
  reg [3:0] w;
  reg [1:0] s;
  wire [3:0] y;

  barrel_shifter bs1(w,s,y);

  initial begin
    w = 1001;
    #10
    s = 00;
    #10
    s = 01;
    #10
    s=10;
    #10
    s=11;
    #20
    $stop;
  end
endmodule

```

Simulation Result:

 

UNIVERSAL BARREL SHIFTER

This does both logical and rotational shifts using mode. Left/right is decided by dir.

We also select shift amount using s.

```
`timescale 1ns / 1ps
```

```
module barrel_shifter_universal(
    input [3:0] w,    // data in
    input [1:0] s,    // shift amount
    input    mode, // 0 = logical, 1 = rotate
    input    dir, // 0 = left, 1 = right
    output [3:0] y    // shifted output
);
    wire [3:0] in0, in1, in2, in3;

    // Generate mux inputs based on mode & direction
    assign in0 = (dir==0) ?
        { w[3], w[0], w[1], w[2] } : // Rotate left by 1
        { w[1], w[2], w[3], w[0] }; // Rotate right by 1

    assign in1 = (dir==0) ?
        { w[2], w[3], w[0], w[1] } : // Rotate left by 2
        { w[2], w[3], w[0], w[1] }; // Rotate right by 2 (same pattern for 4 bits)

    assign in2 = (dir==0) ?
        { w[1], w[2], w[3], w[0] } : // Rotate left by 3
        { w[3], w[0], w[1], w[2] }; // Rotate right by 3

    // Select inputs for logical shift mode
    wire [3:0] log_shift [3:0];
    assign log_shift[0] = (dir==0) ? { w[2:0], 1'b0 } : { 1'b0, w[3:1] }; // shift by 1
    assign log_shift[1] = (dir==0) ? { w[1:0], 2'b00 } : { 2'b00, w[3:2] }; // shift by 2
    assign log_shift[2] = (dir==0) ? { w[0], 3'b000 } : { 3'b000, w[3] }; // shift by 3
```

```

// Final selection based on mode
wire [3:0] sel0 = (mode) ? in0 : log_shift[0];
wire [3:0] sel1 = (mode) ? in1 : log_shift[1];
wire [3:0] sel2 = (mode) ? in2 : log_shift[2];


// Multiplex based on shift amount
assign y = (s == 2'b00) ? w :
           (s == 2'b01) ? sel0 :
           (s == 2'b10) ? sel1 :
           sel2;


endmodule


`timescale 1ns / 1ps


module tb_barrel_shifter_universal;


    reg [3:0] w;
    reg [1:0] s;
    reg     mode; // 0 = logical, 1 = rotate
    reg     dir;  // 0 = left, 1 = right
    wire [3:0] y;


    // Instantiate DUT
    barrel_shifter_universal uut (
        .w(w),
        .s(s),
        .mode(mode),
        .dir(dir),
        .y(y)
    );


    integer i, j, k;

```

initial begin

// Test with an easy-to-see pattern

w = 4'b1011;

// Loop through all modes (0 = logical, 1 = rotate)

for (i = 0; i < 2; i = i + 1) begin

mode = i;

// Loop through both directions (0 = left, 1 = right)

for (j = 0; j < 2; j = j + 1) begin

dir = j;

// Loop through shift amounts (0 to 3)

for (k = 0; k < 4; k = k + 1) begin

s = k;

#10; // wait 10ns between each case

end

end

end

\$stop;

end

endmodule